


**CS2100 Computer Organisation**  
**Tutorial #9: Sequential Circuits**  
 (Week 11: 1 – 5 April 2024)  
**Answers**

**Discussion Questions:**

D1. The state table on the right describes the state transition of a circuit with 4 states *A*, *B*, *C* and *D*, an input *x*, and an output *z*. For example, if the circuit is in state *A* and its input *x* is 0, then it moves into state *C* and generates the output 0 for *z*.

	<i>x</i>	
	0	1
<i>A</i>	<i>C</i> /0	<i>A</i> /1
<i>B</i>	<i>D</i> /1	<i>B</i> /0
<i>C</i>	<i>B</i> /1	<i>D</i> /0
<i>D</i>	<i>C</i> /0	<i>D</i> /0

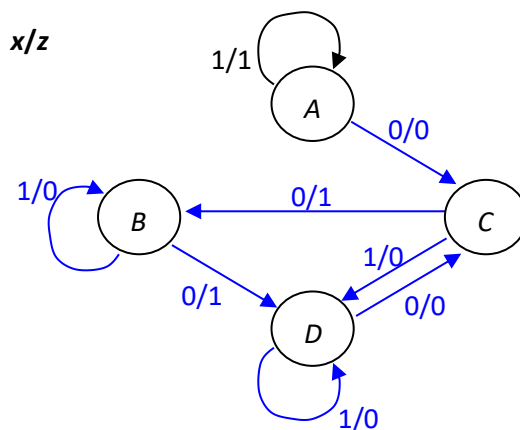(a) Complete the state diagram below. The label of the arc indicates input/output, hence 1/1 means *x*=1 and *z*=1.




(b) Assuming that the circuit starts in state *A*, find the output sequence and state sequence for the input sequence *x* = 100010 (read from left to right). (*x* = 100010 means that initially *x* is 1, then in the next clock *x* is 0, and so on.)


State *Q*:        *A*   *A*   *C*   *B*   *D*   *D*  
 Input *x*:        1   0   0   0   1   0  
 Next state *Q*<sup>+</sup>: *A*   *C*   *B*   *D*   *D*   *C*   ← required answer  
 Output *z*:        1   0   1   1   0   0   ← required answer

D2. Match the following state diagrams to the 4 flip-flops: *JK* flip-flop, *D* flip-flop, *RS* flip-flop, and *T* flip-flop. Don't-care value is indicated by "x".


(a) *D* flip-flop

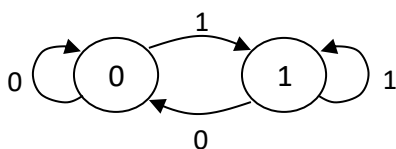


(b) *SR* flip-flop

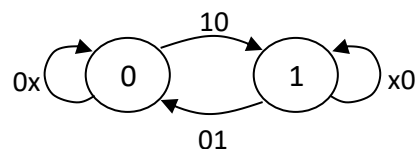

(c) *T* flip-flop

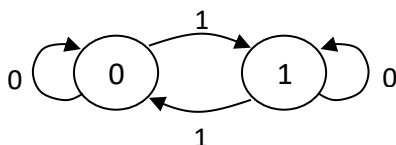


(d) *JK* flip-flop

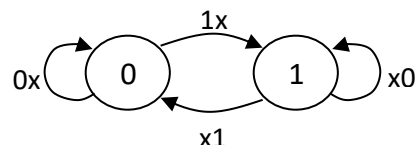

## Tutorial Questions

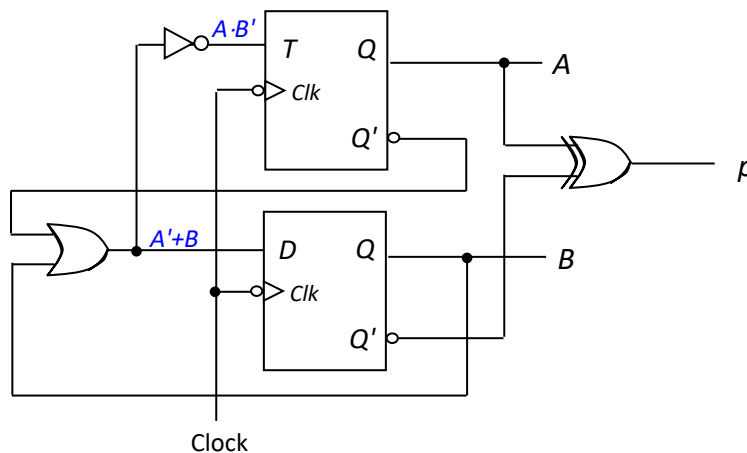1. A four-state sequential circuit below consists of a **T flip-flop** and a **D flip-flop**. Analyze the circuit.



- (a) Complete the state table and hence draw the state diagram.  
 (b) Assuming that the circuit is initially at state 0, what is the final state and the outputs generated after 3 clock cycles?

A state is called a **sink** if once the circuit enters this state, it never moves out of that state.


- (c) How many sinks are there for this circuit?  
 (d) Which is likely to be an unused state in this circuit?

**Answers:**

(a)

$$\begin{aligned} p &= A \cdot B + A' \cdot B' \\ TA &= A \cdot B' \\ DB &= A' + B \end{aligned}$$


Present state		Output	Flip-flop inputs		Next state	
A	B	p	TA	DB	A+	B+
0	0	1	0	1	0	1
0	1	0	0	1	0	1
1	0	0	1	0	0	0
1	1	1	0	1	1	1

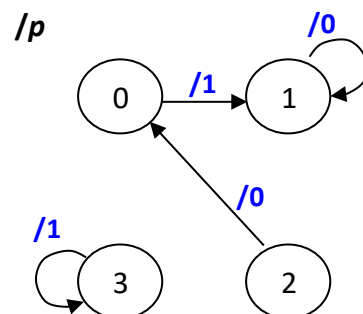


- (b) After 3 clock cycles, the circuit is in state 1, and it generated 100 as output.  
 (c) There are 2 sinks: states 1 and 3.  
 (d) State 3 is likely to be an unused state.

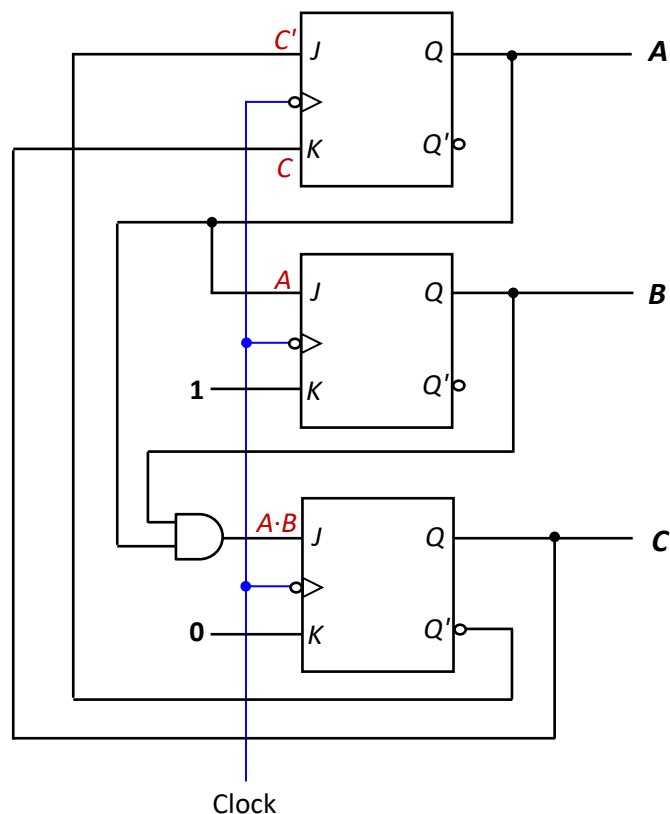2. [AY2021/22 Semester 2 Exam]

A sequential circuit with 6 states: state 1 ( $ABC=001_2$ ) through state 6 ( $ABC=110_2$ ) is implemented using three JK flip-flops as shown below.



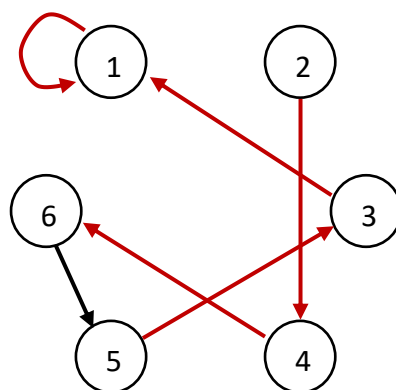(a) Complete the state diagram below. One of the transitions has been drawn for you.



(b) A circuit is **self-correcting** if for some reason the circuit enters into any unused (invalid) state, it is able to transit to a valid state after a finite number of transitions. Is this circuit self-correcting? Explain.

**Answer:** Yes, it is self-correcting. State 0 transits to state 4 and state 7 transits to state 1.


Working:

(a)  $JA = C'$ ;  $KA = C$ ;  $JB = A$ ;  $KB = 1$ ;  $JC = A \cdot B$ ;  $KC = 0$ .

Fill in the flip-flop inputs in the state table using the above expressions, then find the values of  $A^+$ ,  $B^+$ , and  $C^+$ .

Present state			Next state			Flip-flop inputs					
A	B	C	A <sup>+</sup>	B <sup>+</sup>	C <sup>+</sup>	JA=C'	KA=C	JB=A	KB=1	JC=A·B	KC=0
0	0	0	1	0	0	1	0	0	1	0	0
0	0	1	0	0	1	0	1	0	1	0	0
0	1	0	1	0	0	1	0	0	1	0	0
0	1	1	0	0	1	0	1	0	1	0	0
1	0	0	1	1	0	1	0	1	1	0	0
1	0	1	0	1	1	0	1	1	1	0	0
1	1	0	1	0	1	1	0	1	1	1	0
1	1	1	0	0	1	0	1	1	1	1	0

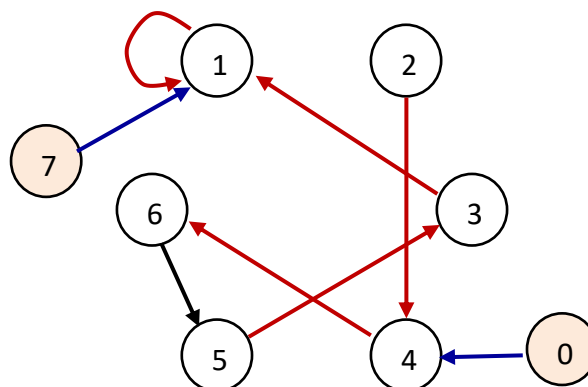State diagram with unused states 0 and 7.



3. [AY2021/22 Semester 2 Exam]

Redesign the circuit in question 2 by using only **T flip-flops**. You do not have to follow where the unused states transit to in question 2. Write out the flip-flop input functions  $TA$ ,  $TB$  and  $TC$  so that your new design can be implemented with the fewest number of logic gates other than the flip-flops.

**Answers:** 3 logic gates (XNOR, OR, AND)

$$TA = A \cdot C + A' \cdot C' = A \odot C$$

$$TB = A + B$$

$$TC = A \cdot B$$

Working:

Present state			Next state			Flip-flop inputs		
A	B	C	A <sup>+</sup>	B <sup>+</sup>	C <sup>+</sup>	TA	TB	TC
0	0	0	X	X	X	X	X	X
0	0	1	0	0	1	0	0	0
0	1	0	1	0	0	1	1	0
0	1	1	0	0	1	0	1	0
1	0	0	1	1	0	0	1	0
1	0	1	0	1	1	1	1	0
1	1	0	1	0	1	0	1	1
1	1	1	X	X	X	X	X	X

**TA**

	B			
	X	0	0	1
A	0	1	X	0

C

**TB**

	B			
	X	0	1	1
A	1	1	X	1

C


**TC**

	B			
	X	0	0	0
A	0	0	X	1

C

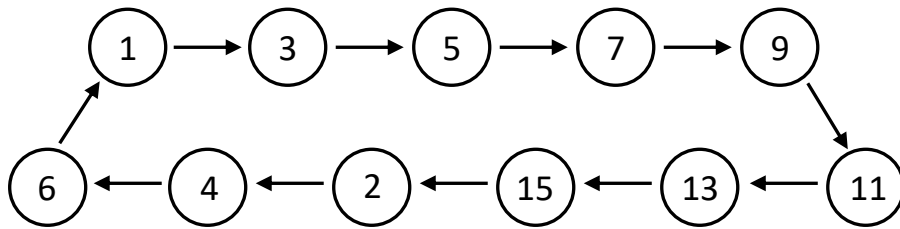
4. [AY2018/19 Semester 2 exam]

A sequential circuit goes through the following states, whose state values are shown in decimal:





The states are represented by 4-bit values  $ABCD$ . Implement the sequential circuit using a  $D$  flip-flop for  $A$ ,  $T$  flip-flops for  $B$  and  $C$ , and a  $JK$  flip-flop for  $D$ .

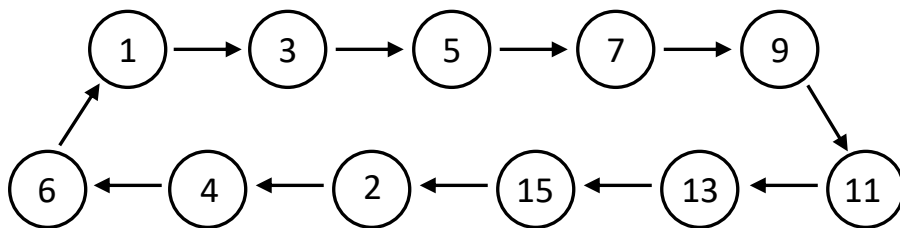- Write out the **simplified SOP expressions** for all the flip-flop inputs.
- Implement your circuit according to your simplified SOP expressions obtained in part (a). Complete the given state diagram, by indicating the next state for each of the five unused states.
- Is your circuit self-correcting? Why?



Answers:

Current state				Next state							
A	B	C	D	DA=A <sup>+</sup>	B <sup>+</sup>	C <sup>+</sup>	D <sup>+</sup>	TB	TC	JD	KD
0	0	0	0	X(0)	X(0)	X(1)	X(0)	X(0)	X(1)	X(0)	X(0)
0	0	0	1	0	0	1	1	0	1	X	0
0	0	1	0	0	1	0	0	1	1	0	X
0	0	1	1	0	1	0	1	1	1	X	0
0	1	0	0	0	1	1	0	0	1	0	X
0	1	0	1	0	1	1	1	0	1	X	0
0	1	1	0	0	0	0	1	1	1	1	X
0	1	1	1	1	0	0	1	1	1	X	0
1	0	0	0	X(1)	X(0)	X(1)	X(0)	X(0)	X(1)	X(0)	X(0)
1	0	0	1	1	0	1	1	0	1	X	0
1	0	1	0	X(1)	X(1)	X(0)	X(0)	X(1)	X(1)	X(0)	X(0)
1	0	1	1	1	1	0	1	1	1	X	0
1	1	0	0	X(1)	X(1)	X(1)	X(0)	X(0)	X(1)	X(0)	X(0)
1	1	0	1	1	1	1	1	0	1	X	0
1	1	1	0	X(0)	X(0)	X(1)	X(1)	X(1)	X(0)	X(1)	X(1)
1	1	1	1	0	0	1	0	1	0	X	1

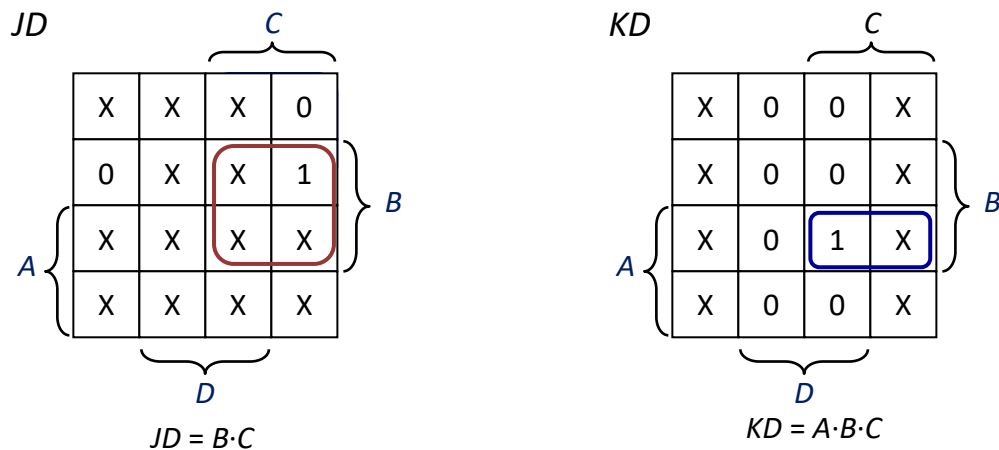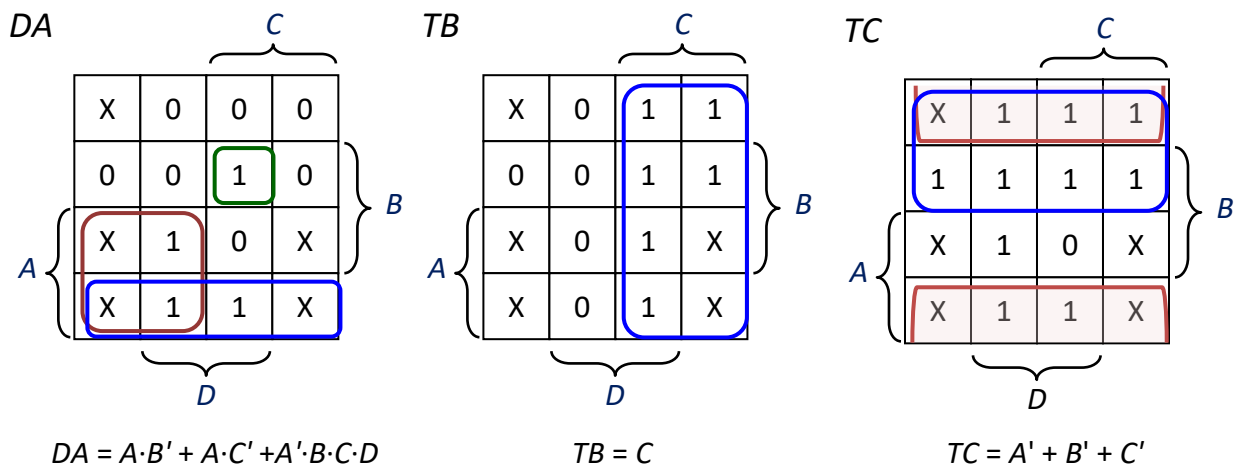


$$DA = A \cdot B' + A \cdot C' + A' \cdot B \cdot C \cdot D$$

$$TB = C$$

$$TC = A' + B' + C'$$

$$JD = B \cdot C$$

$$KD = A \cdot B \cdot C$$

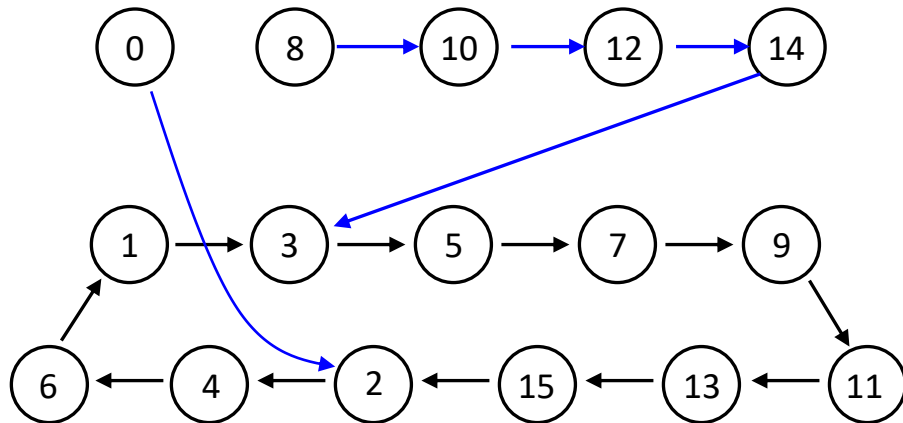

The circuit is self-correcting as any unused state can transit to a used state after a finite number of cycles.